



## Lab 10 - Analog to Digital and Digital to Analog Conversion

University of California at Berkeley

Donald A. Glaser Physics 111A

Instrumentation Laboratory

### Lab 10

#### Analog to Digital and Digital to Analog Conversion

©2015 by the Regents of the University of California. All rights reserved.

#### References: <sup>[1]</sup>

[The Art of Electronics](#), <sup>[2]</sup> Horowitz & Hill Chapter 13.

[Other References](#) <sup>[3]</sup>

#### Physics 111-Lab Library Reference Site

Reprints and other information can be found on the [Physics 111 Library Site](#). <sup>[4]</sup>

**NOTE: You can check out and keep the portable breadboards, VB-106 or VB-108, from the 111-Lab for yourself ( Only one each please)**

In this lab you will learn how to convert data between analog and digital, and the many pitfalls in doing so.

Several LabVIEW programs are mentioned in this lab writeup. Many of these programs can be downloaded from the **111lab\BSC Share\ on the U: Drive from the 111-Lab computers**. Two versions of the programs are typically available for download: an executable version that should run without LabVIEW (but requires a large download from National Instruments, which should occur automatically, and only needs to be done once) and should run on PC's, Mac's and Linux boxes; and the original LabVIEW source code which requires LabVIEW.

#### Before coming to class complete this list of tasks:

- Completely read this Lab Write-up
- Answer the pre-lab questions utilizing the references and this write-up
- Perform any circuit calculations use [MatLab](#) <sup>[5]</sup> or anything that can be done outside of lab [RStudio](#) <sup>[6]</sup> (freeware).
- Begin and if possible complete programming tasks in this lab write-up
- Plan out how to perform Lab exercises in this write-up.

All parts spec sheets are located on the [Physics 111 Library site](#). <sup>[1]</sup>

#### Prelab

---

1. Given the DAC in Exercise 10.2 has a resolution of 5 bits, how close to their ideal values must each resistor be?
  2. Assuming that the DAQ digital output high level is exactly 5V, what is the full scale value (largest output) of the DAC in this exercise?
- 

## Background:

### Digital representation of numbers

Our world is largely analog and continuous; quantities vary smoothly. There are, of course, intrinsically discrete exceptions to this rule, like the quantization of charge or the quantum hall effect. But even measurements of discrete phenomena tend to be confounded by noise and produce continuous data. Internally, however, modern computers<sup>[1]</sup> deal only with discrete quantities; specifically, they deal only with quantities take on only two values: on or off. This so-called digital representation of information has many advantages over analog representations, most importantly that digital information is relatively immune to noise. If a 0, or off state, is represented by a voltage near 0, and a 1, or on state is represented by a voltage near 4 (a scheme used by a common family of digital devices called TTL logic), then noise is unlikely to cause a fluctuation great enough to confuse the two.

Because computers can only represent two states, numbers are stored in binary, or base 2. The digits in a base 2 number are called bits, thus, a typical number in base 2 number is a collection of bits like 01011010. Numbers are decoded using a power series in 2:

$$\sum_{n=0}^{\infty} a_n 2^n = a_0 2^0 + a_1 2^1 + a_2 2^2 + a_3 2^3 + \dots$$

where the  $a_n$  are the series of bits used to represent the number. Thus,

Base 10	0	1	2	3	4	5	6	7
Base 2	000	001	010	011	100	101	110	111

The more bits used, the larger the integer number that can be represented. Non-integer numbers are represented by multiplying in an appended exponent; thus, the more bits, the greater the precision of the number.

Eight bits taken together constitute a byte, and computers are typically organized around byte processing, not bit processing.

### Conversion

Since the real world is analog, but the computer world is binary, we need to be able to convert signals between the two. Devices that change an analog signal to a digital signal are called analog to digital converters (ADC). Devices that change a signal the other way, from digital to analog, are called digital to analog converters (DAC). Both are important; DACs are used to control experiments, while ADCs are used to read data from experiments.

### Sampling


Real-world signals are continuous in time as well as level. Thus, to represent a time-varying signal, we build up a table of the value of the signal as a function of time, for example:

Time	Signal
0	1.000
0.125	0.649
0.250	-0.156

0.375	-0.853
0.500	-0.951
0.625	-0.383
0.750	0.454
0.875	0.972
1.000	0.809
1.125	0.078
1.250	-0.707
1.375	-0.997
1.500	-0.588
1.625	0.233
1.750	0.891
1.875	0.924
2.000	0.309

These values are called samples.

 We can better visualize sample tables with a graph. The curve in upper plot of the graph below represents a signal to be sampled. The dots are the samples. If we then use the samples to represent the signal, we get the signal in the lower plot, where the points are joined by the dashed line.



Sampling always approximates the signal. How accurate is the representation? There are two basic limits on the accuracy, resolution and sampling rate.

## Resolution

The number of bits available to represent each sample is called the resolution. In base 2, the number of levels that can be represented by an  $n$  bit sample is  $2^n$ . Thus, for 8 bits (the number of bits in a typical low end converter) there are 256 levels, while for 24 bits (the maximum common[2] converter resolution) there are 16,777,216 levels.

It is rare that we would need precisions better than 1 part in 1000, or 10 bits. What then is the point of going to higher resolution? Higher resolution provides greater range. It is uncommon for the signal amplitude to exactly match the full-scale value of the converter. Typically, we might have a margin of over a factor of ten; perhaps 4 bits. Thus, to get 10 bit accuracy we would need a 14 bit converter.

Even if the maximum amplitude of our signal matches the full-scale value of the converter, the signal amplitude is likely to vary significantly over time. (This is called “dynamic range.”) For instance, the sound level from a symphony orchestra varies from about 40dB to 130dB. (Sounds at 130dB are rare; the “cannon” in the Tchaikovsky’s 1812 overture are one example.) Consequently, the amplitude of the sound waves varies by a factor of about 30,000. This seemingly requires about 15 bits. But with 15 bits, the lowest levels would be represented by just one bit level changes. A sine wave represented by only one bit becomes a square wave. We would prefer to better represent low signals; perhaps six bits for the lowest levels. Thus, we would need a 21 bit converter to well represent the signal.[3] However, CDs use only 16 bits.[4] To record symphonic music without distortion, engineers typically compress the signal; the quietest passages are made louder, while the loudest passages are softened.

A higher resolution also makes it easier to extract signals from noise. Say we are using a 10 bit ADC to digitize a small signal which is masked by noise whose level is 10 bits. We could not amplify the signal because the noise would cause our converter to saturate. You might think that the signal would have to be larger than one bit to be detected. Curiously, if there were no noise, this would be true. But with noise, we can detect signals which are smaller than one bit.[5] Still, it’s much better not to have to rely on the noise to make the signal measurable, and we would be better off with a higher precision ADC.


## Sampling Rate

The effects of the sampling too slowly are more subtle than the effects of limited resolution. When we sample too slowly, we do not get an adequate representation of the signal; in fact, we may be badly confused by spurious signals. These effects were codified by Nyquist, who determined that:


A signal can only be perfectly represented by a samples taken at more than twice the maximum frequency in the signal.

Thus if we sample at rate  $f_s$ , then the signal must contain no information with frequencies higher than  $f_s/2$ . This latter frequency is called the Nyquist Frequency.

 
If we violate Nyquist’s theorem we get aliasing; signals at higher frequencies get shifted down to lower frequencies. For example, if we have a sinusoidal signal with frequency 1Hz, and sample it at frequency 10.4Hz, we get a good representation of the signal (but note that the peaks are still slightly distorted.)



 But if we sample the signal below the minimum sample frequency for this wave of 2 Hz, we get an aliased signal. For instance, if we sample the signal at a frequency of 1.7 Hz we get:




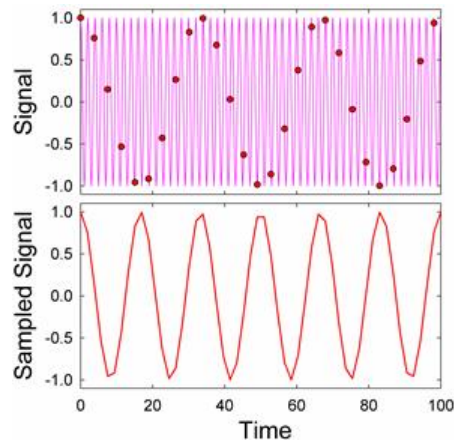In this case, we get a garbage signal, and we might well guess that the signal has been aliased. But sometimes we get seemingly good signals, as in this case where we sample at a frequency of 0.53Hz:



It is very easy to confuse a signal like this one for a real signal. We need to be very careful when interpreting a sampled signal.

While aliased signals can look quite confused, it is quite easy to understand the origin of aliasing in frequency space. Signals above the Nyquist frequency do not simply vanish; they get mirrored[6] into frequencies below the Nyquist frequency. Thus, if we sample a signal that has desired frequency content below the Nyquist frequency (shown in green in the diagram below) and undesired “noise” about the Nyquist frequency (shown in pink), the undesired signal will be reflected around the Nyquist Frequency into the midst of the desired signal.

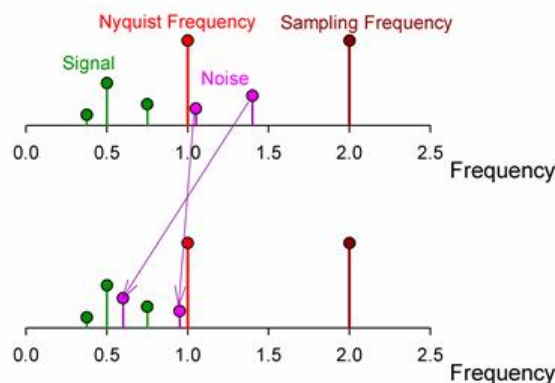

The location of the mirrored, or aliased, signals is easy to predict:


$$\begin{aligned}
 f_{Observed} &= f_{Nyquist} - ( f_{Actual} - f_{Nyquist} ) \\
 &= f_{Sample} - f_{Actual}
 \end{aligned}$$

Actually, this is only the first of the mirrored frequencies. Signals are mirrored again and again<sup>5</sup> like in a barbershop mirror. But each time they get mirrored, their amplitude decreases, so we typically ignore all but the first mirror.

 
## Picking a Sample Frequency

It is always safest and easiest to pick a sampling frequency well above the highest anticipated frequency. A factor of ten to hundred times higher provides a comfortable margin. But there are times when it is not feasible to pick such a high frequency. Your converter may be incapable of sampling fast enough, or the desired rate may be technologically infeasible. Even if a converter with the desired sample rate exists, it may be prohibitively expensive; the cost of ADCs and DACs increase rapidly with sampling speed. For instance a 250kS/s (kilo Sample/sec) ADC costs just 375 today (2005) : a 10MS/s card costs 4000, and a 1GS/s card costs \$10,000. And then, even if you do have an appropriately fast card, you may find that the fast data rate overwhelms your system, and you may be forced to sample slower anyway.


Nyquist's theorem states that you need only sample at twice the desired frequency. What happens if you are close to the Nyquist limit? The sampled signal may not appear to resemble the actual signal. For instance, if you sample a sine wave at 2.35 times its frequency, you get:



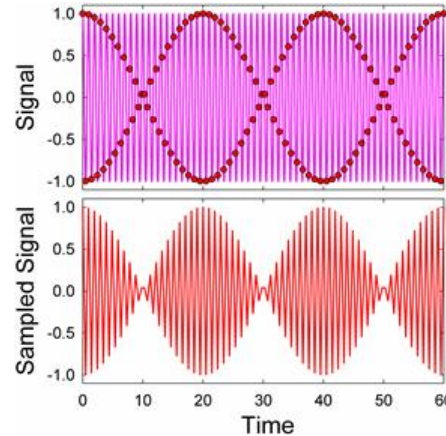
Sampling at 2.05 times the frequency yields:



 
Neither sampled signal resembles the original signal. Is Nyquist wrong? Comparing the spectrum of the original signal to the sampled signal illuminates the problem:



The original signal contains one clean peak at the original frequency. The sampled signal has an extra peak at a frequency a bit higher than the original.[8] The amplitude modulations in the sampled signal are due to these two peaks in the sampled spectrum beating against each other. We can largely recover the original frequency by low-pass filtering the sampled signal to destroy the spurious peak:

 


Unfortunately, filtering is not always easy to accomplish. It is relatively easy to filter a signal on a computer by taking its Fourier transform and discarding the spectral content about the Nyquist frequency. But filtering with real-world components in real time is not nearly so easy. A simple one pole RC filter does not roll off fast enough, so we need to cascade filters to make them roll off faster:

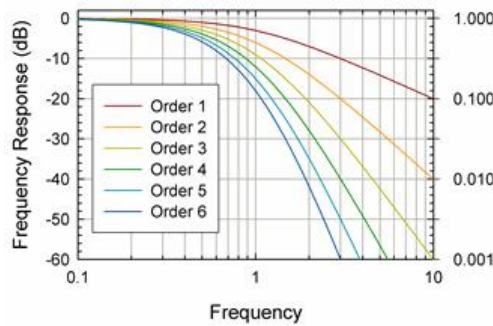


The 6<sup>th</sup> order RC filter depicted above rolls off quite fast; its transfer function is down by two orders of magnitude one octave about its design corner at 1Hz. But it has also significantly reduced the signal amplitude in the passband below 1. Signal aliasing may not be a problem, but the original signal will be distorted.

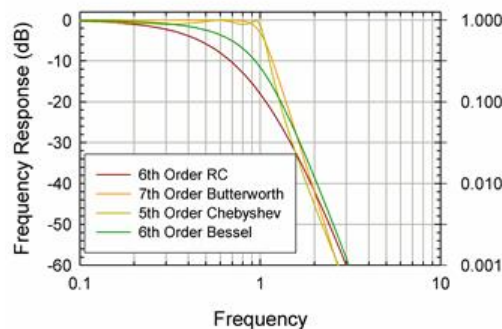Filter design is an exceedingly complicated topic, and there are better filters exist than simple RC designs. Typical advanced designs are called Butterworth, Chebyshev, and Bessel filters, and their response is plotted below.




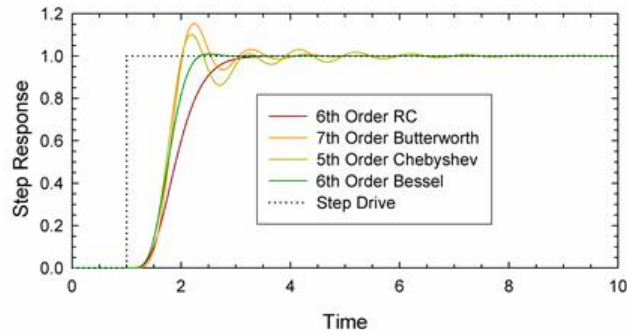The order of the filters have been adjusted so that they attenuate by a factor of 100 one octave about their design frequency of 1Hz. The Butterworth and Chebyshev filters look very attractive; they cut off quickly, but leave the pass-band relatively unmodified. Unfortunately, their transient response is poor. Feed a step into them, and the will distort the signal:






All the filters delay the onset of the step, and The Butterworth and Chebyshev filters ring significantly. The Bessel filters has the best step response, but its frequency response is not as good as the Butterworth and Chebyshev filters. In sum, perfect filters cannot be constructed outside of a computer. Even in a computer, it is difficult to make a perfect filter. The spectrum of the signal sampled at 2.05 contains one major spurious peak above the Nyquist frequency, but is also contains smaller spurious peaks below the Nyquist frequency. These peaks distort the signal. For instance, if we sample a signal consisting of two equal amplitude sine waves at frequencies of 0.7 and 1, at a sampling frequency of 3, we can do a fair job of reconstructing the original signal:

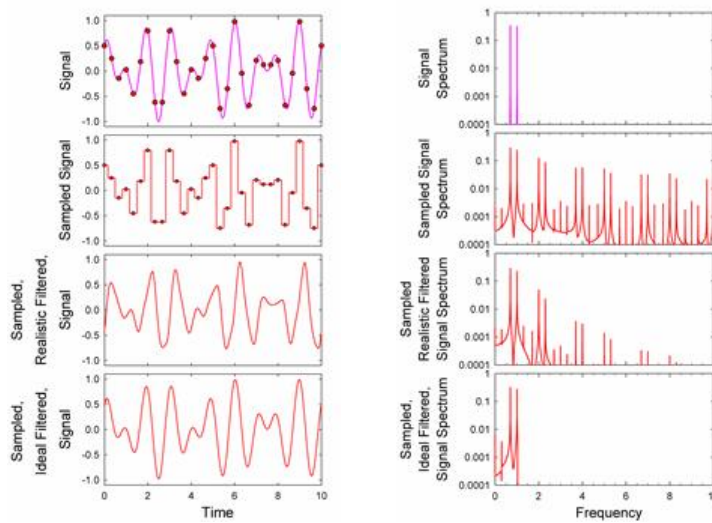


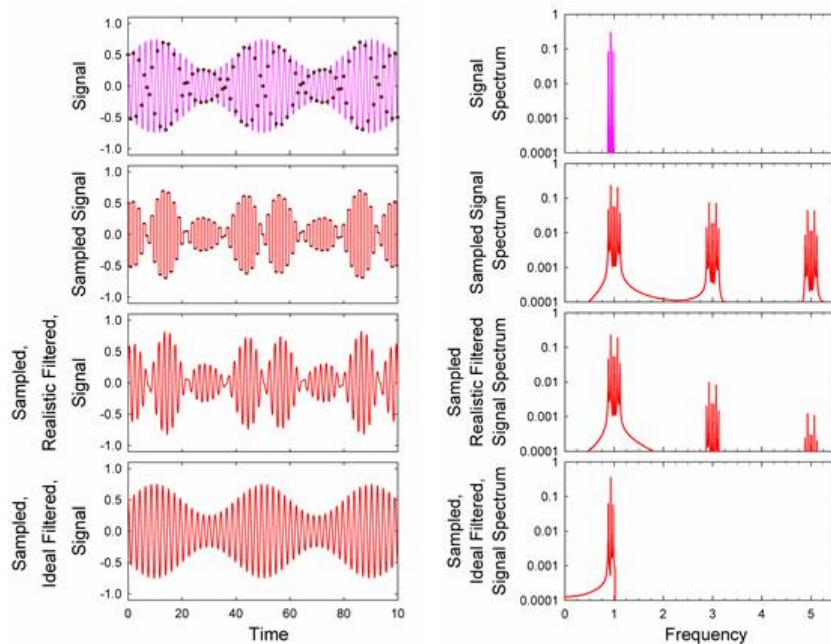Nonetheless, the spectrum shows many spurious peaks, whose effects are visible on careful comparison with the original signal. With the ideal, computer filter, however, the spectrum is much closer to the original signal spectrum and differences to the original signal are insignificant. The effects of imperfect filtering are even more visible for an AM modulated carrier wave:








 One should remember that the sampled signal is just a table of values. When we plot the sampled data, we need to interpolate between the sampled points. There are several ways to interpolate. Starting from uninterpolated data:



   
we can step interpolate (used on most DACs), ramp interpolate (used on some expensive DAQs) or comb interpolate.




Comb interpolation, which uses a sequence of infinite delta functions, each with area equal to the amplitude of sample at successive points, is difficult to use in the real world, because delta functions are unphysical. Surprisingly though, it is theoretically optimal, as can be seen from the proof of Nyquist's theorem, [http://en.wikipedia.org/wiki/Nyquist\\_theorem](http://en.wikipedia.org/wiki/Nyquist_theorem) [7]
 
## Digital to Analog Converters

There are several ways to build digital to analog converters, but the simplest way is with a scaled resistor network:



This is just an Op-Amp adder circuit, in which each bit's  $b_n$  is added in with weight  $2^{b_n}$ . In practice, it is difficult to make a high resolution DAC with a scaled resistor network because it requires precisely scaled resistors over a very wide range. It is much easier to make precise resistors over a narrow range; [9] a common DAC that takes advantage of this fact uses a ladder network:

 

Like the scaled resistor ADC, this circuit also adds together appropriately weighted bits.

## Practical Filtering and Aliasing Advice

ADCs: Always make sure that you are not being fooled by aliasing artifacts. The best way to test for the presence of artifacts is to look at the signal with your entire detector, amplifier, and ADC chain in place and adjusted to your contemplated settings, but with your experiment turned off so that you are receiving no real data. If you observe a significant signal, you then know that you are observing an artifact.


- Occasionally, the received signal is so free of noise that aliasing of unwanted frequencies is unimportant. If so, either: (1) sample at twenty or more times the desired signal frequency, or (2) sample closer to twice the desired signal frequency and use digital filtering to remove the artifacts.
  - The maximum frequency of most received signals is naturally limited by the detector that produced the signal, or by the detector amplifiers. If possible, sample at a frequency that is higher than twice the maximum frequency of the received signal, using digital filtering, as necessary, to remove the artifacts.
- If the desired signal is centered around a narrow band of frequencies, you may be able to ignore aliasing artifacts. Set your ADC to sample at several times the band center frequency. Establish that you can ignore aliasing artifacts by the test described above, concentrating only on signals in the band of interest. If you do observe artifacts, you may be able to get rid of them by changing your sample frequency so that the spurious signals alias to a different frequency that is out of your band of interest.
- In necessary, employ a filter to remove the high frequency noise. Some ADCs come with anti-aliasing filters built-in. These are filters are likely to be quite good; use them before building your own. Otherwise, use your own anti-aliasing filter. If you can, use a simple RC low-pass filter designed to cut off at a much higher than your signal frequency, (so that the pass-band attenuation at the signal frequency is small) and sample at a frequency much higher than the filter's cut off frequency (so that the filter attenuation is large above the Nyquist frequency.) If you cannot space your cutoff and sample frequency so generously, obtain a commercial filter, or, if all else fails, build a sophisticated multipole filter optimized for your application.

## DACs:

- If your DAC and memory can support it, use a sample frequency 20 to 200 times greater than your signal frequency.
- The device you are driving may not care about spurious high frequency components. In this case, you can run quite close to the Nyquist frequency without filtering.
- If your signal is close to the Nyquist frequency, use a filter. Some DAC's come with high quality filters; use them if available. Otherwise, use a commercial filter, or a simple RC filter. If your signal is close to a pure sine wave, and you can tolerate variations in its amplitude with frequency, you may be able to generate relatively undistorted signals quite close to the Nyquist frequency.
- If nothing else works, design a higher order filter optimized for your signal.
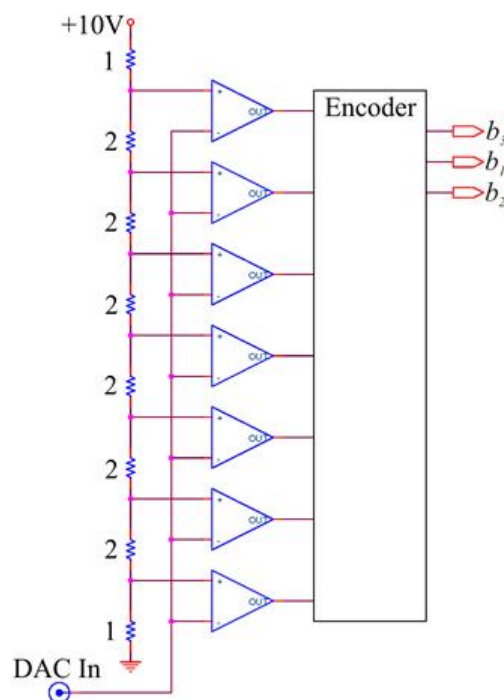
## Analog to Digital Converters

The simplest way to make an n-bit ADC is to have  $2^n$  separate comparators, each comparing the input voltage to one of the set of all the voltage levels allowed by the resolution of the ADC:




An encoder determines the highest "on" comparator, and encodes this information into a number. Such flash, or parallel recorders are very fast, and are used in high frequency applications. But they are not feasible for high resolution ADCs, as every voltage level requires a separate comparator.

Conversion is more commonly done by a successive approximation ADC. This type of ADC successively refines a guessed value in a loop. The steps in the loop are:

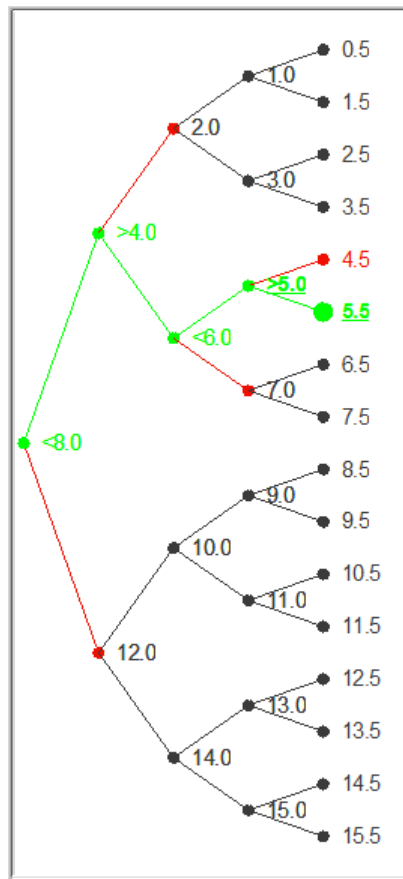1. Convert the guess to a voltage using a DAC.
2. Compare this guess voltage to the input voltage.
3. Refine the guess:
  - a. If the guess is too low, make a new guess that is higher. The new guess should be half way between the current guess and the last known guess that was too high.
  - b. If the guess is too high, make a new guess that is lower. The new guess should be half way between the current guess and the last known guess that was too low.
4. Begin the cycle again if the conversion has not exhausted all the DAC bits. Otherwise, call the final guess the answer and end the loop.

The loop is initialized by setting the last known limits to be the minimum and maximum values accepted by the ADC, and setting the

first guess to be half way in between. This process is best illustrated by a tree diagram, shown here for an ADC whose range is 0 to 16V:



Here the input signal is 5.3. In the first loop iteration the ADC guesses that the answer is 8, and compares this guess with 5.3. Since 5.3 is less than the guess, the ADC refines the guess to be half as big: namely 4. This guess is smaller than the input, so the ADC refines its guess on the next loop to be 6, half way between 4 and 8. Six is too large, so the next guess is 5, half way between 4 and 6. Finally the best guess is determined to be 5.5, half way between 5 and 6, because 5 is less than 5.3.

Successive approximation methods are as accurate as their internal DAC. They can be quite fast, as they can chase down an n bit tree in n steps, giving  $2^n$  resolution. For increased speed, some DACs combine flash converters and successive approximation converters. The flash converts are used to quickly find the highest order bits, perhaps the first 5, and successive approximate used to find the remaining bits. There are many other techniques as well; manufacturers aggressively develop improved devices.

### In the lab



### Problem 10.1 - Aliasing and Sample Rate

Open the file *U:\BSC Share\LAB\_10\Lab Stations\Sampling\_Simulator.llb*, and then run *Sampling Simulator.vi* from the LLB Manager. With filtering set to **No Filter**, explore the effects of the sample rate on **Pure Sine** and **Square** waves. Use both **Flat Interpolation** and **Linear Interpolation**. In your lab notebook, record your answers to the following questions:

1. Sample a 1Hz, phase 90 **Sine** wave at 4Hz. Do you get a reasonable facsimile of the original sine wave? Now change the phase. What happens? Do you still get a reasonable facsimile? Restore the phase to 90. What happens when you change the sample rate to 4.01? Can you account for the difference?
2. Repeat these measurements with a **Square** wave, and record your answers.
3. Using a 1Hz **Sine** wave, try some inadequate sampling rates, say 1.9, 1, 0.9, 0.5 and 0.47Hz. Can you account for the features you observe?
4. Explore the effects of inadequate sampling rates on a **Square** wave.

5. What sample rate is necessary to give a reasonable facsimile of a sine wave, and what sample rate gives a reasonable facsimile of a square wave? Why are these frequencies different?
6. Now find appropriate sample rates for the **Two Tone, AM**, and **FM** signals. Ironically, you may conclude that these signals can be sampled at a lower rate than the pure sine wave. This is probably because these signals are so complex that the sampling artifacts so clearly visible with the **Sine** signal are masked.
7. Now try the **Realistic Low Pass Filter** with the **Sine** signal and various sample rates. Can you employ lower sample rates? Look at the amplitude as well as the form of the sampled and filtered signals. Is the amplitude sometimes incorrect even when the form is correct?
8. Look at **Square** waves with the **Realistic Low Pass Filter**. What is the effect of the sample rate? Using the **Expanded Time Axis**, cycle between **Realistic Low Pass Filter** and **No Filter**. Note that the filter causes the rise and falls to be delayed. What is the size of the delay? Does it depend on the sample rate? Note that the realistic filter is a 3<sup>rd</sup> order Butterworth. Does this fact explain the delay?
9. Look at the **Two Tone, AM**, and **FM** signals. Does the filter help?
10. Now go back to a 1Hz **Sine** wave, and set the sample rate to just above 2Hz, say 2.1Hz. Does any interpolation method produce a reasonable facsimile of the wave with the **Realistic Low Pass Filter**? (Hint: Ask what is reasonable?) Switch to the **Ideal Low Pass Filter**. Is it better? What do your signals look like for the different interpolations? Which one gets the amplitude correct? With **Comb Interpolation**, how low a sample frequency can you use? Try sample rates of 2.02 and 2.01Hz. In principle, you should be able to go down to 2.00Hz, but, in practice, 2.01Hz has problems. Can you explain why? (This is hard and is not obvious from the material covered in this writeup or in lecture.)
11. Now go to a sample rate of 1.95Hz. Is the **Ideal Low Pass Filter** any better than the **Realistic Low Pass Filter**?
12. With the **Ideal Low Pass Filter** and **Comb Interpolation**, explore sampling ranges above 2.00Hz for the **Two Tone, AM**, and **FM** signals. How good are the sampled signals? Try a **Square Wave**? Why is the sampled signal no good?


Show and discuss your results to the TA's.

---

## Problem 10.2 - Digital to Analog Conversion


---

Build a scaled resistor DAC:

 



Use the digital outputs<sup>[10]</sup> of your DAQ card to drive the outputs; in particular, use the low order bits marked P0.0 (lowest) to P0.4. These digital outputs switch between approximately 0 and +5V; consequently your converter will output negative voltages. You will have to scale your resistors up from the values used in the above schematic; determine the base value (the "1") from the requirement that the current drawn from any of the digital outputs individually should be less than 2.5mA. We do not have the precise resistor values that you will need. You will have to synthesize the correct values by combining two or more resistors.

 Correct your Pre-Lab Question calculation of the full scale voltage of the DAQ by measuring the actual high level output of the DAQ.<sup>[11]</sup> Build a LabVIEW driver for your DAC.<sup>[12]</sup> Your driver's front panel should look something like:




where the Bit Pattern indicator is included for debugging purposes. You will have to scale the output voltage to a bit pattern. LabVIEW already has Vis for many common tasks such as this, try to find the right one for the job before you implement your own (Try searching “Boolean array”). You should make sure that you cannot drive your DAC with an out-of-range bit pattern. A

convenient way to assure that you don't is to use LabVIEW's *In Range and Coerce* operator,  which can be found amongst the comparison operators menu. Use your scope or multimeter to test your DAC. Note that even though you are driving the digital lines with one byte (actually only 5 bits in one byte) of data, the *DAQ Assistant* expects an array. Use the *Build Array* operator  to turn your byte into a one element array of bytes.

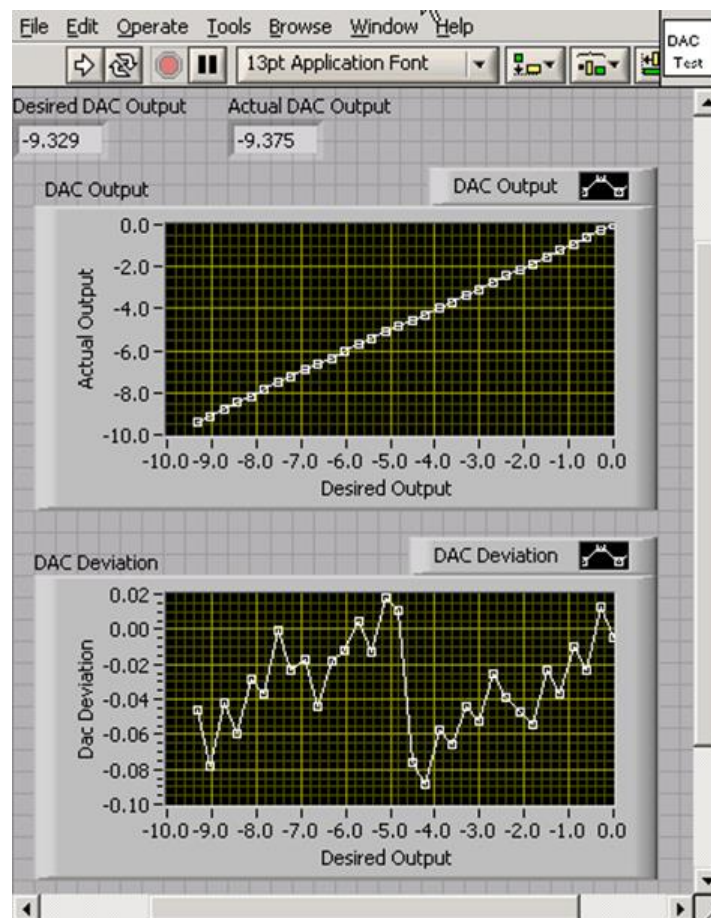
### Problem 10.3

Write a program to test your DAC.<sup>[13]</sup> The program's front panel should look something like



The program should:

1. Loop through all of the possible DAC output levels.
2. At each level

- a. Display the Desired DAC output with an indicator.
  - b. Drive the DAC
    - c.  Wait twenty milliseconds for the DAC to settle. Use the *Wait* operator found under Time and Dialog Operators menu.
  - d. Read the output of the DAC with one of the analog input channels of the DAQ.
- Hint: Use a Stacked Sequence Structure for steps b-d
- e. Output the DAC voltage.
    - i. Display the DAC output with an indicator.
    - ii. Store the current Desired Output and Actual Output in an array and use an XY plot to display a graph of the Desired Output vs. the Actual Output. The best way to do this is with shift registers. The program *Running XY Graph Example* demonstrates the technique.
- Hint: Also use Build Arrays and the Bundle functions. If you're having trouble, be sure to review the Array section of the LabVIEW Basics I tutorial.
- iii. Subtract the Desired Output from the Actual Output to find the DAC Deviation, and display a running graph.


Explain the systematic features in the DAC Deviation graph. What is the maximum error? Demonstrate your program and the DAC Driver SubVI to the TA's and explain their block diagrams.

---
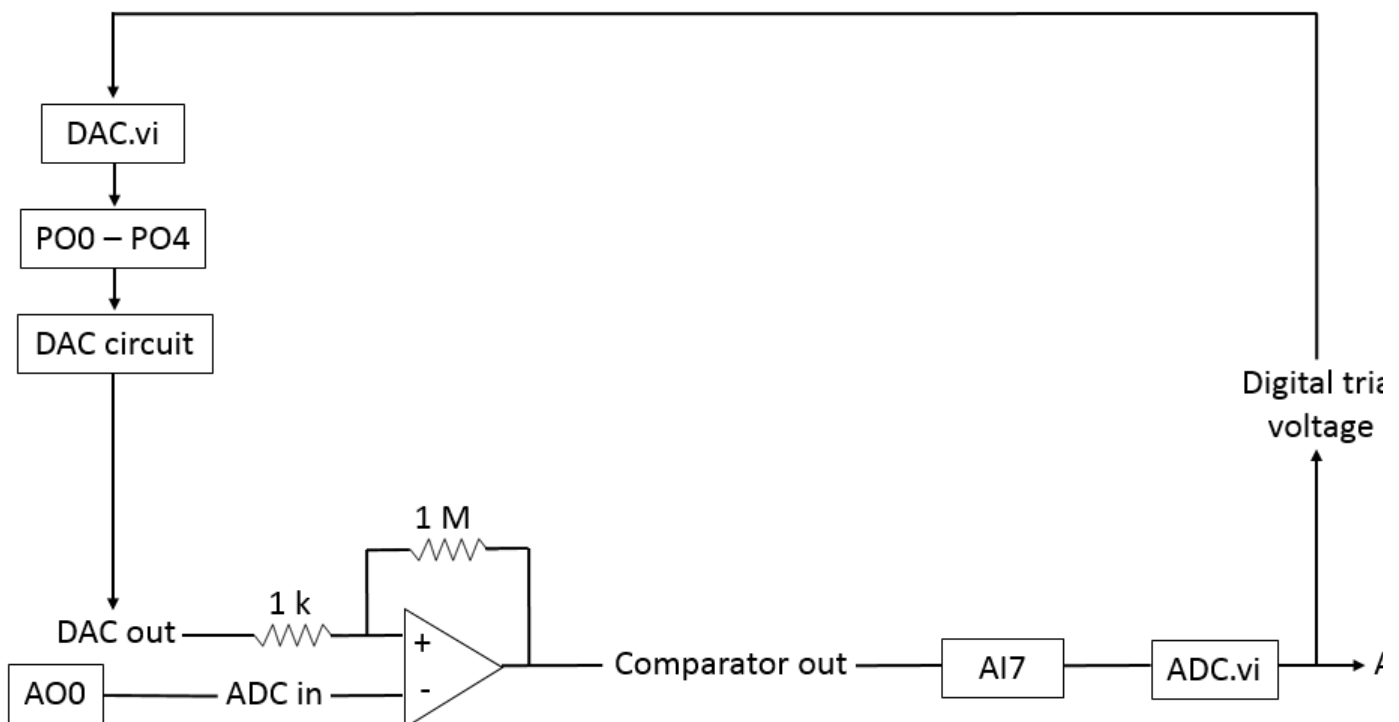
### Problem 10.4 - Analog to Digital Conversion

---

Build a successive approximation ADC by adding a comparator to your DAC:



[8]


Write the following programs to complete the ADC implementation:

 1. *Compare Trial.vi*. This subroutine should accept a **Trial Voltage**, write it to the DAC, wait 10ms for the DAC to settle, measure the output voltage of the comparator, and compare this voltage to some fixed voltage to determine if the **Trial Voltage** is greater than or less than the **ADC Input Voltage**. The front panel of the vi should look




something like:

*Hint:* Again, The Stacked Sequence Structure works well for timing control.



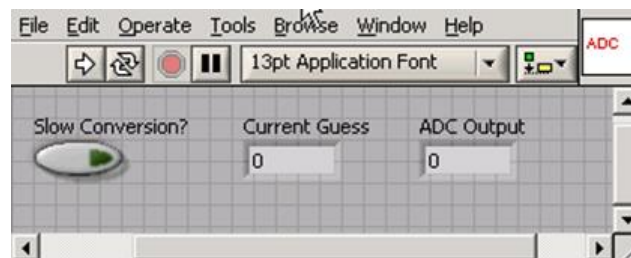2. *ADC.vi*. This routine should guess successive **Trial Voltage**'s until the ADC converges. You may find it helpful to organize your iterations in a for loop, remembering the previous high and low guesses from iteration to iteration with shift registers, Also Case Structures and Expression Nodes are helpful. For debugging purposes, you might wish to put in an indicator giving the current guess, and a switch controlling a 1s per iteration delay. Your front panel should look something like:




To help you get started, working versions of these programs are available on the lab computers. The block diagrams of these programs are inaccessible. You may also use the program *Set Voltage to be Converted* to set precise voltages on the DAQ analog output channel AO-0.

---
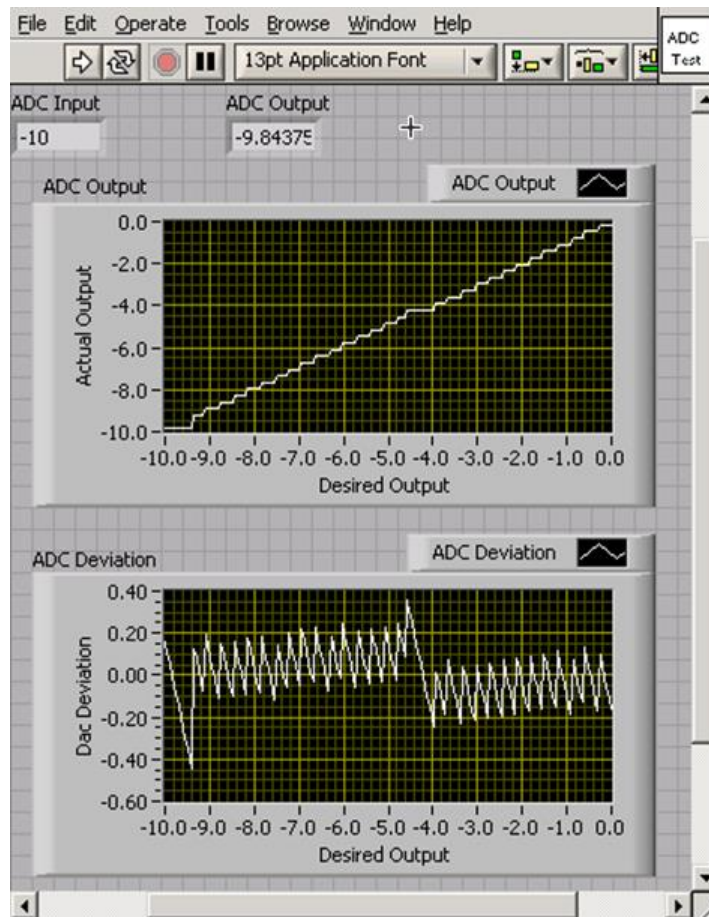
## Problem 10.5

---

Write a program to test the ADC. The program should be similar to your DAC tester except that it should convert an essentially continuous voltage ramp. The front panel of the program should look something like:



Explain the systematic features in the ADC Deviation graph. What is the maximum error? Demonstrate your program and its SubVIs to the TA's, and explain their block diagrams.

---

### Problem 10.6

---

The routine *Test DAQ ADC and DAC.vi* is very similar to the *Test ADC* routine that you just wrote, but tests the DAC and ADC of the DAQ. After attaching the AO-0 output to the AI-7 input, run the routine to test the accuracy of the DAQ converters. The DAQ DAC and ADC are both 16 bit converters. How big is a 1bit error? Are any of the errors larger than one bit?

Note: The output on the front panel of *Test DAQ ADC and DAC.vi* that outputs the number of errors larger than 1 bit is incorrect - you should figure this out on your own. We'll fix the software as soon as permission issues are resolved.

---

### Problem 10.7 - Filtering

---

Use the program *Sine DAQ Drive.vi* to output a 5V sine wave on AO-0. The sample rate is 10kHz. The drive frequency is adjustable; look at the output on a scope for a range of frequencies. (Don't exceed the Nyquist frequency.) About when is the signal acceptable? Now use 3.3k resistors to construct simple low pass filters with cut off frequencies near 10kHz and 1kHz. Drive the filters with the output from the DAQ. Draw pictures of the waveforms, and determine when the signal is acceptable. Note both amplitude changes and phase delays.

---

### Student Evaluation of Lab Report

---

[1] Originally, computers were analog, and did computations in ways similar to the way that you did computations in your RMS converters. Programming was done by wiring patch panels, as can be seen in the photos of the analog computers below.

 


Plate 13 (a). Analogue computer system designed by E.M.I.  
Electronics as a simulator for studying complex control problems  
associated with guided weapons.

[2] The National Instruments PXI-4461, available for a mere \$3995.

[3] In principle, using floating point numbers (a mantissa and an exponent) would better represent the music. But floating point converters are difficult to make and very rare. After the signal is sampled, however, one can convert the numbers to floating point without much loss of information. This is one of the tricks used in compressing music in schemes like mp3s.

[4] The program *Wave\_Quantization* illustrates the effects of resolution on an audible signal.

[5] The technique of deliberately adding noise to a signal to reduce the effects of quantization is called dithering: see <http://en.wikipedia.org/wiki/Dither> [10]

[6] The program *Whistle\_Aliasing* audibly demonstrates mirroring, including the effects of multiple mirroring.

[7] The program *Wav\_Aliasing* audibly demonstrates the effects of aliasing on a music sample.

[8] More precisely, signals mirror up as well as down around the Nyquist frequency, so the frequency of the second peak is at 1.05.

[9] Precision resistors can be fabricated over a narrow range by a technique called laser trimming, in which a laser is used to etch away small sections of the resistive material while monitoring the total resistance. Laser trimmed resistors made on the same chip are particularly precise, and will also track together as the temperature changes.

[10] The digital lines are available on your interface box as screw terminals. Strip about ¼ inch of insulation from a wire, push it into the rectangular hole, and gently tighten the screw below. Do not overtighten, and make sure that you use the correct screw driver.

[11] You may find it helpful during this exercise to drive the digital lines with the DAQ's debugging interface. Open the *DAQ Assistant* for the DAQ, configure it for digital output, and go to the Test tab.

[12] The program *DAC.vi* implements this functionality, and you may use it to get started. You will not be able to access its block diagram.

[13] The program *Test\_DAC.vi* implements this functionality, and you may use it to get started. You will not be able to access its block diagram.

---

**Source URL:** <http://instrumentationlab.berkeley.edu/Lab10>

#### Links

[1] <http://physics111.lib.berkeley.edu/Physics111/BSC/indexbsc.html>

[2] <http://physics111.lib.berkeley.edu/Physics111/BSC/Readings/Horowitz&Hills%20Books/indexHorowitz.html>

[3] <http://physics111.lib.berkeley.edu/Physics111/BSC/Readings/indexreadings.html>

[4] <http://physics111.lib.berkeley.edu/Physics111/>

[5] <http://instrumentationlab.berkeley.edu/matlabintro>

[6] <https://www.rstudio.com/products/rstudio/features/>

[7] [http://en.wikipedia.org/wiki/Nyquist\\_theorem](http://en.wikipedia.org/wiki/Nyquist_theorem)

[8] [http://instrumentationlab.berkeley.edu/sites/default/files/BSC10/ADC\\_diagram.PNG](http://instrumentationlab.berkeley.edu/sites/default/files/BSC10/ADC_diagram.PNG)

[9] <http://instrumentationlab.berkeley.edu/StudentEvaluation>

[10] <http://en.wikipedia.org/wiki/Dither>